

Written Test for Degree Engineering Interview

Date: 20/07/2024 Time: 1 hr

Marks: 20

Note: All questions carry equal marks

1. If silicon diode is operating in forward bias in a circuit with 12 V supply and $240\ \Omega$ series resistance, then what is the voltage drop across the diode.
A. 1.5 V B. 0.4 V C. 1.1 V D. 0.7 V
2. In feedback control system shown in Figure 1 below $G(s) = \frac{6}{s(s+1)(s+2)}$, where $R(s)$, $Y(s)$, & $E(s)$ are Laplace transform of $r(t)$, $y(t)$, & $e(t)$ respectively, if the input $r(t)$ is a unit ramp function then ———
A. $\lim_{t \rightarrow \infty} e(t) = 0$ B. $\lim_{t \rightarrow \infty} e(t) = \frac{1}{3}$ C. $\lim_{t \rightarrow \infty} e(t) = \frac{1}{4}$ D. $\lim_{t \rightarrow \infty} e(t)$ does not exist, $e(t)$

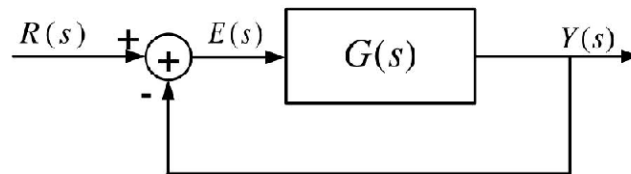


Figure 1: Q.No.2

is oscillatory.

3. What is the z-transform of the following finite duration signal? $x[n] = \{2, 4, 5, 7, 0, 1\}$
A. $2 + 4z + 5z^2 + 7z^3 + z^4$ B. $2 + 4z + 5z^2 + 7z^3 + z^5$ C. $2 + 4z^{-1} + 5z^{-2} + 7z^{-3} + z^{-5}$
D. $2z^2 + 4z + 5 + 7z^{-1} + z^{-3}$
4. The BJT as a switch is operated in one of the following: A. Only saturation region
B. Active region C. Only cut off region D. Both saturation and cut off region
5. A DC power supply has no load voltage of 30 V and full load voltage of 25 V at full load current of 1 A. Its output resistance and load regulation respectively are.
A. $5\ \Omega$ and 20% B. $25\ \Omega$ and 20% C. $5\ \Omega$ and 16.7% D. $25\ \Omega$ and 16.7%
6. A 500 W carrier signal is amplitude modulated modulation percentage of 60%. The total power in the modulated signal if the form amplitude modulation used is the double sideband AM with full carrier (A3E).
A. 590 W B. 534 W C. 125 W D. 300 W

7. What will be the o/p of the given logic gate of Figure 2?

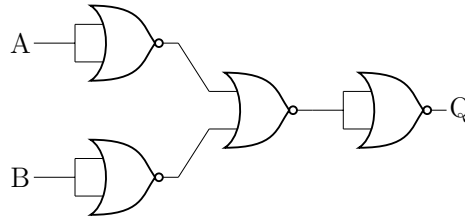


Figure 2: Q.No.7

A. NOR B. NAND C. AND D. OR

8. Let \hat{i} and \hat{j} be the unit vectors along x and y axes respectively, and let A be the positive constant. Which one of the following is true for vector fields $\vec{F}_1 = A(\hat{i}y + \hat{j}x)$, $\vec{F}_2 = A(\hat{i}y - \hat{j}x)$

A. Both \vec{F}_1 and \vec{F}_2 are electrostatic fields. B. Only \vec{F}_1 is an electrostatic fields.
C. Only \vec{F}_2 is an electrostatic fields. D. Neither \vec{F}_1 nor \vec{F}_2 are electrostatic fields.

9. The current I_y flowing through 660Ω resistance is (Refer Figure 3):

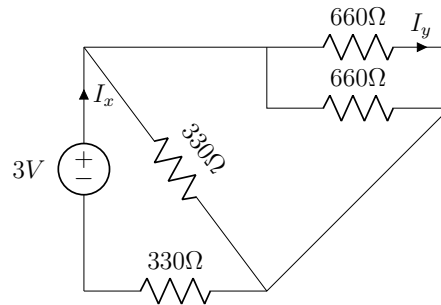


Figure 3: Q.No.9

A. I_x B. $I_x/2$ C. $I_x/4$ D. $I_x/3$

10. In the circuit shown below, P and Q are the inputs. The logical function realized by the circuit shown Figure 4 below is:

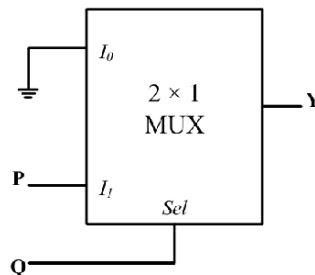


Figure 4: Q.No.10

A. $Y = PQ$ B. $Y = P + Q$ C. $Y = \overline{PQ}$ D. $Y = \overline{P + Q}$