

Tech Nexus Competition 2023-24

Organized by IETE Student Forum, DIET, Satara

Date: 07/03/2024

Time: 10 Min

Marks:10

1. The current I_y flowing through 660Ω resistance is (Refer Figure 1):

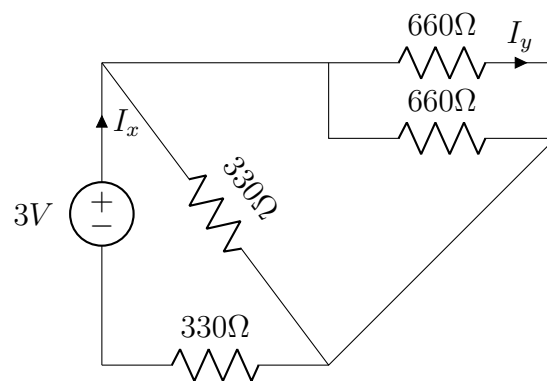


Figure 1: Q.No.1

- A. I_x B. $I_x/2$ C. $I_x/4$ D. $I_x/3$

2. The voltage across 660Ω resistance is (refer Figure 2):

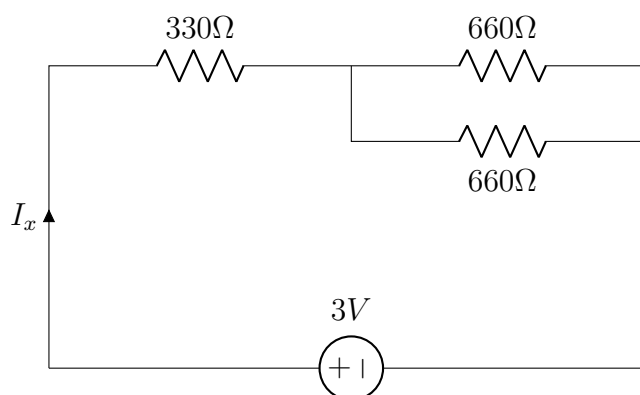


Figure 2: Q.No.2

- A. $0.65V$ B. $1.5V$ C. $0.72V$ D. $0.75V$

3. The current I_x and I_y are (refer Figure 3).

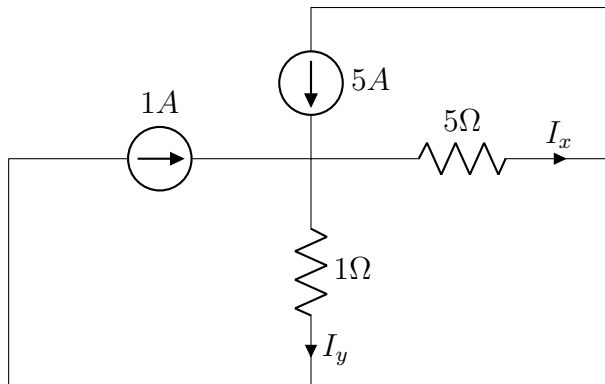


Figure 3: Q.No.3

- A. $-1A, 5A$ B. $5A, 1A$ C. $1A, 5A$ D. $5A, -1A$

4. The current I_1 and I_2 of the circuit shown in Figure 4 are giving by:

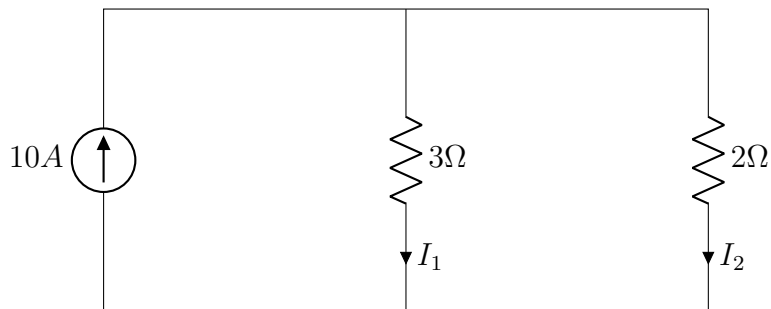


Figure 4: Q.No.4

- A. $4A, 4A$ B. $6A, 6A$ C. $4A, 6A$ D. $6A, 4A$

5. Referring to the circuit of the Figure 5, a $35V$ source is connected to a series circuit of 600Ω and R . If a voltmeter of internal resistance $1.2k\Omega$ is connected across 600Ω , it reads $5V$. The value of R is

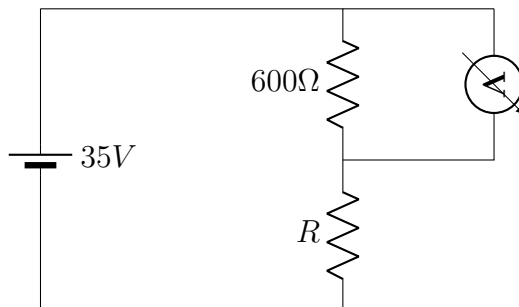


Figure 5: Q.No.5

- A. $1.2k\Omega$ B. $2.4k\Omega$ C. $1.4k\Omega$ D. $3.4k\Omega$

6. The equivalent resistance of the circuit given in Figure 6 is given by


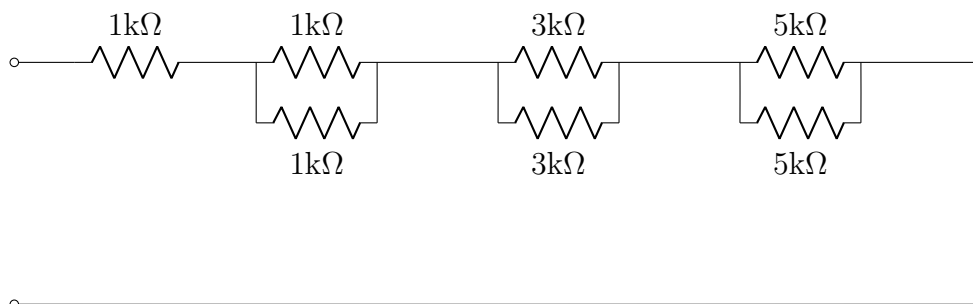


Figure 6: Q.No.6

- A. $4k\Omega$ B. $10k\Omega$ C. $5.5k\Omega$ D. $5k\Omega$

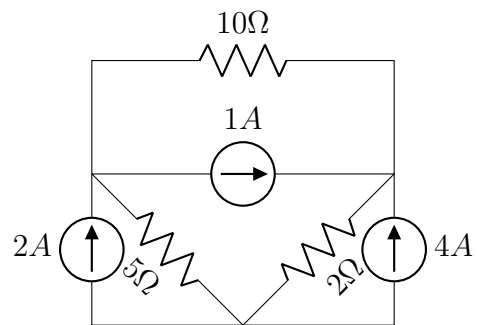7. Find current I , (refer Figure reffig:7).



- A. $\frac{17}{12}$ B. $\frac{11}{17}$ C. $\frac{12}{17}$ D. $\frac{17}{11}$