

Spring 2018  
**Precalculus' Final Examination**  
nth Semester  
Section 000

**Objective:** Assess understanding of function behavior and calculus readiness. This exam also aims to provide a comprehensive assessment on concepts and definitions that are necessary to be successful in further Mathematics courses.)

**General Instructions:** Read carefully each exercise. Fill in your *scantron* with a pencil and circle the correct answer on paper as well. Scratch paper is not allowed under any circumstances. All your work must be done in these pages.

- You have up to 120 minutes.
- Every item on the test awards 2 points for each correct answer, for a maximum possible score of 100 points.
- Non-graphing calculators are allowed. TI-84 or similar, including smart devices, are prohibited.
- One half-page formula sheet printed in black ink and showing the instructor's authorization may be used. Any other form of aid is not allowed.
- Mere suspicion of cheating, sharing calculators or using any unfair means of aid is enough to get your test withdrawn.
- When you are done, turn in the examination, your *scantron* and your formula sheet. Failure to do so will result in an automatic failing grade.

SIDE A

Part I. NETWORK THEORY QUESTIONS.

---

1. The current  $I_y$  flowing through  $660\Omega$  resistance is (Refer Figure 1):

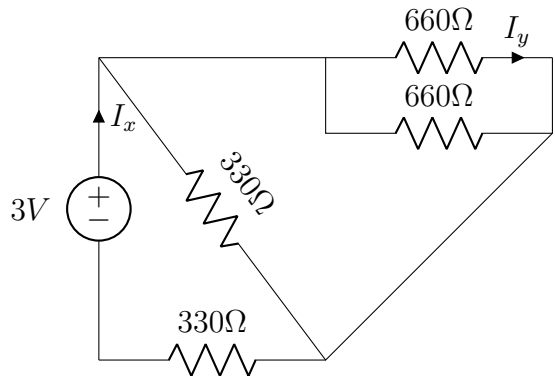


Figure 1: Q.No.1

- A.  $I_x$    B.  $I_x/2$    C.  $I_x/4$    D.  $I_x/3$
2. The voltage across  $660\Omega$  resistance is (refer Figure 2):   A.  $0.65V$    B.  $1.5V$    C.  $0.72V$

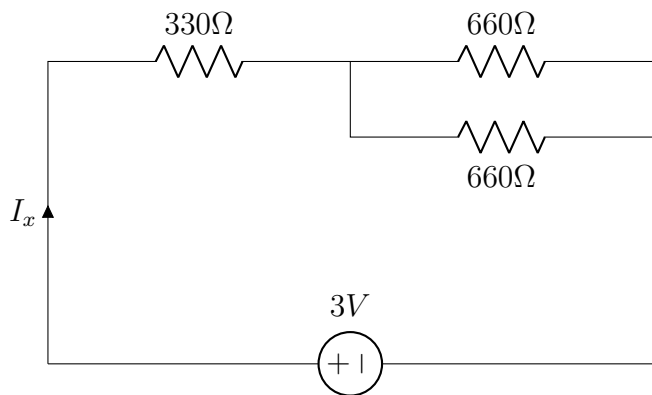


Figure 2: Q.No.2

- D.  $0.75V$
3. The current  $I_x$  and  $I_y$  are (refer Figure 3).   A.  $-1A, 5A$    B.  $5A, 1A$    C.  $1A, 5A$

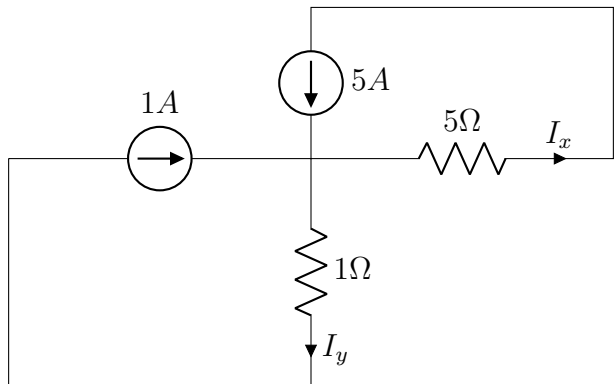


Figure 3: Q.No.3

- D.  $5A, -1A$
4. The current  $I_1$  and  $I_2$  of the circuit shown in Figure 4 are giving by:   A.  $4A, 4A$   
B.  $6A, 6A$    C.  $4A, 6A$    D.  $6A, 4A$
5. Referring to the circuit of the Figure 5, a  $35V$  source is connected to a series circuit of  $600\Omega$  and  $R$ . If a voltmeter of internal resistance  $1.2k\Omega$  is connected across  $600\Omega$ , it reads  $5V$ . The value of  $R$  is   A.  $1.2k\Omega$    B.  $2.4k\Omega$    C.  $1.4k\Omega$    D.  $3.4k\Omega$

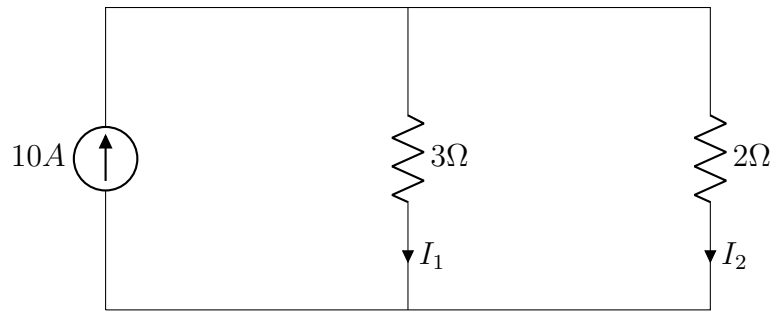


Figure 4: Q.No.4

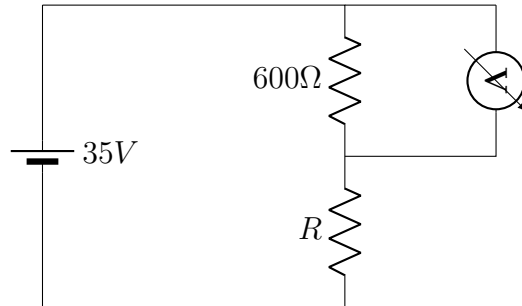


Figure 5: Q.No.5

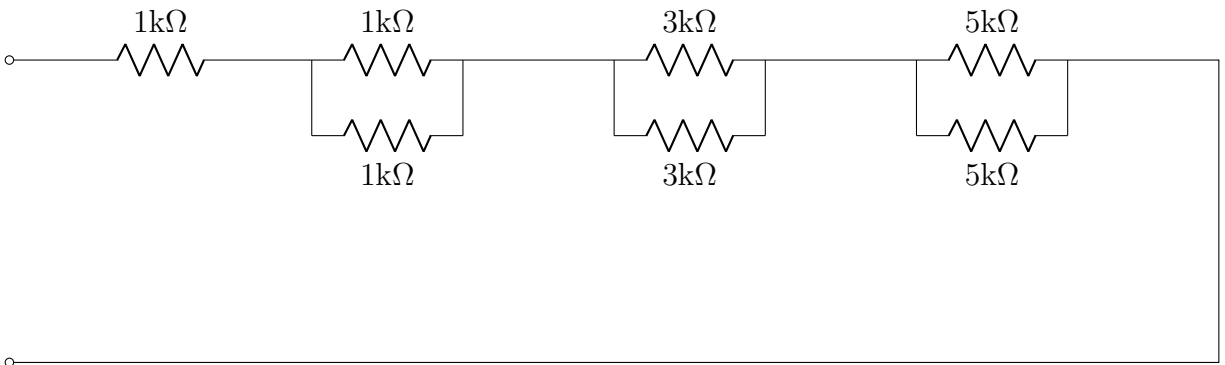


Figure 6: Q.No.6

6. The equivalent resistance of the circuit given in Figure 6 is given by A. 4 kΩ B. 10 kΩ  
C. 5.5 kΩ D. 5 kΩ